

INDUSTRIAL TRAINING ARDUINO & IT'S INTERFACING WITH INTERNET OF THINGS - IOT

The logo for Shreeji Charan Electronics features the word "shreeji" in a large, red, stylized font with a white outline and a drop shadow. Below it, the words "CHARAN ELECTRONICS" are written in a smaller, blue, sans-serif font with a white outline and a drop shadow. The entire logo is set against a yellow background.

Presented by

Chauhan Keyur & Sagar Patel


Electronics and Communication System

Email: shreejicharanelectronics@gmail.com

URL: www.shreejicharanelectronics.com


Serial Communication Interfacing

Different Types of Interfaces

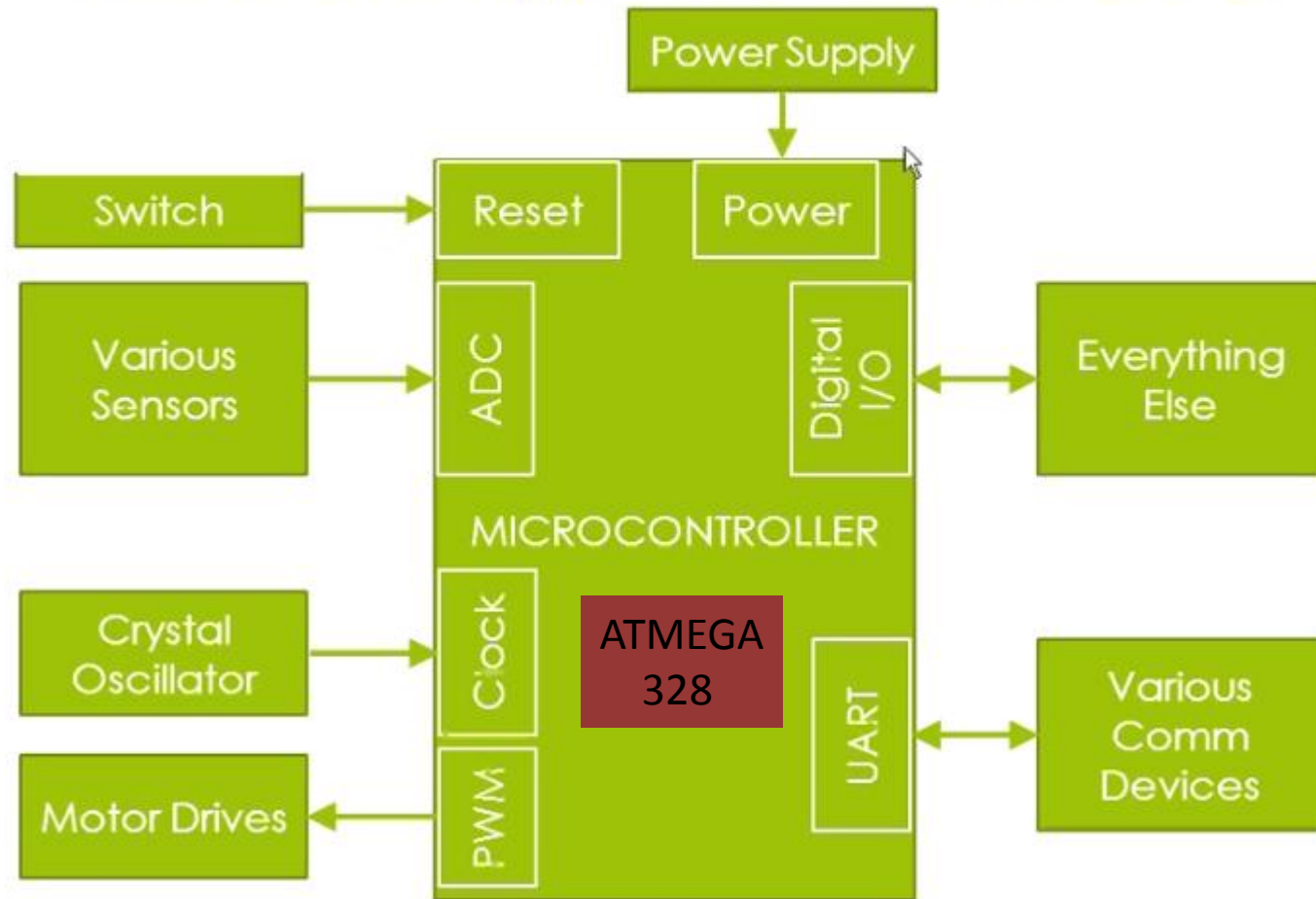


Next >> Minimum Basic Ckt

Power Supply, Clock, Reset

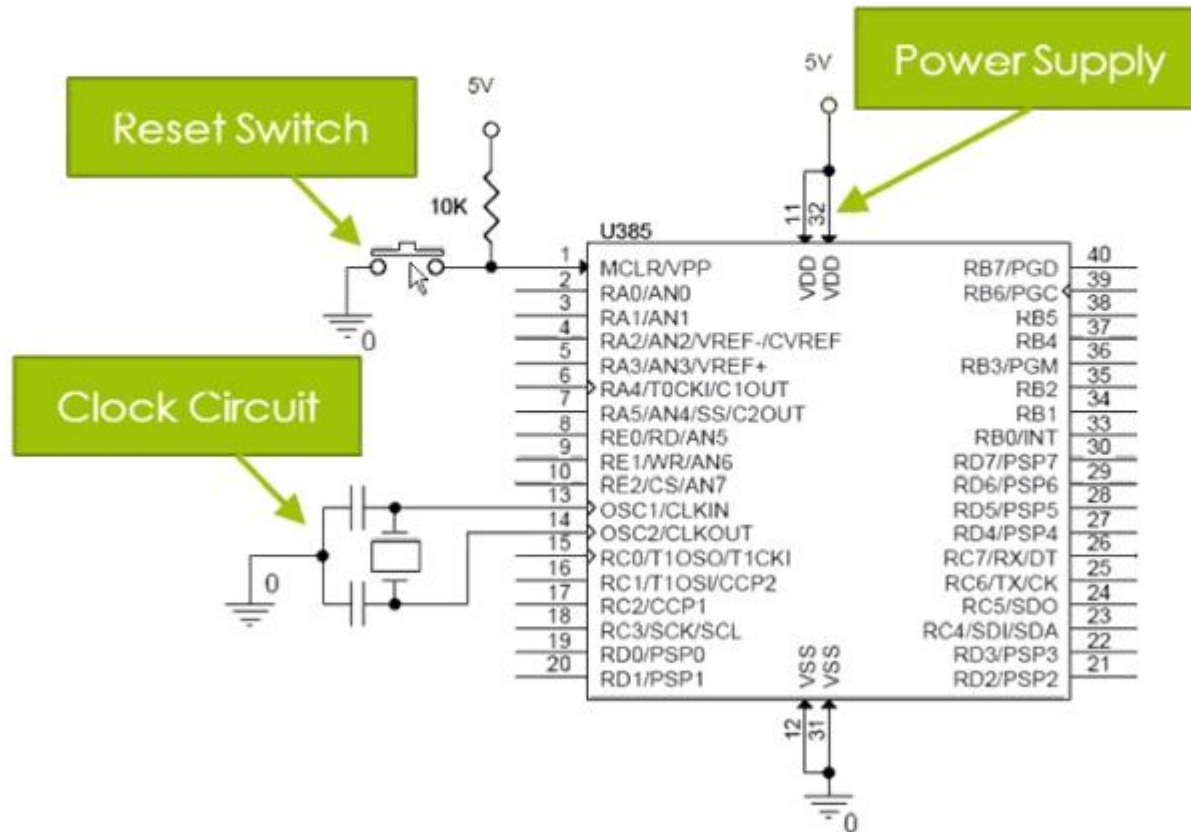


Next >> UART Communication

UART Communication

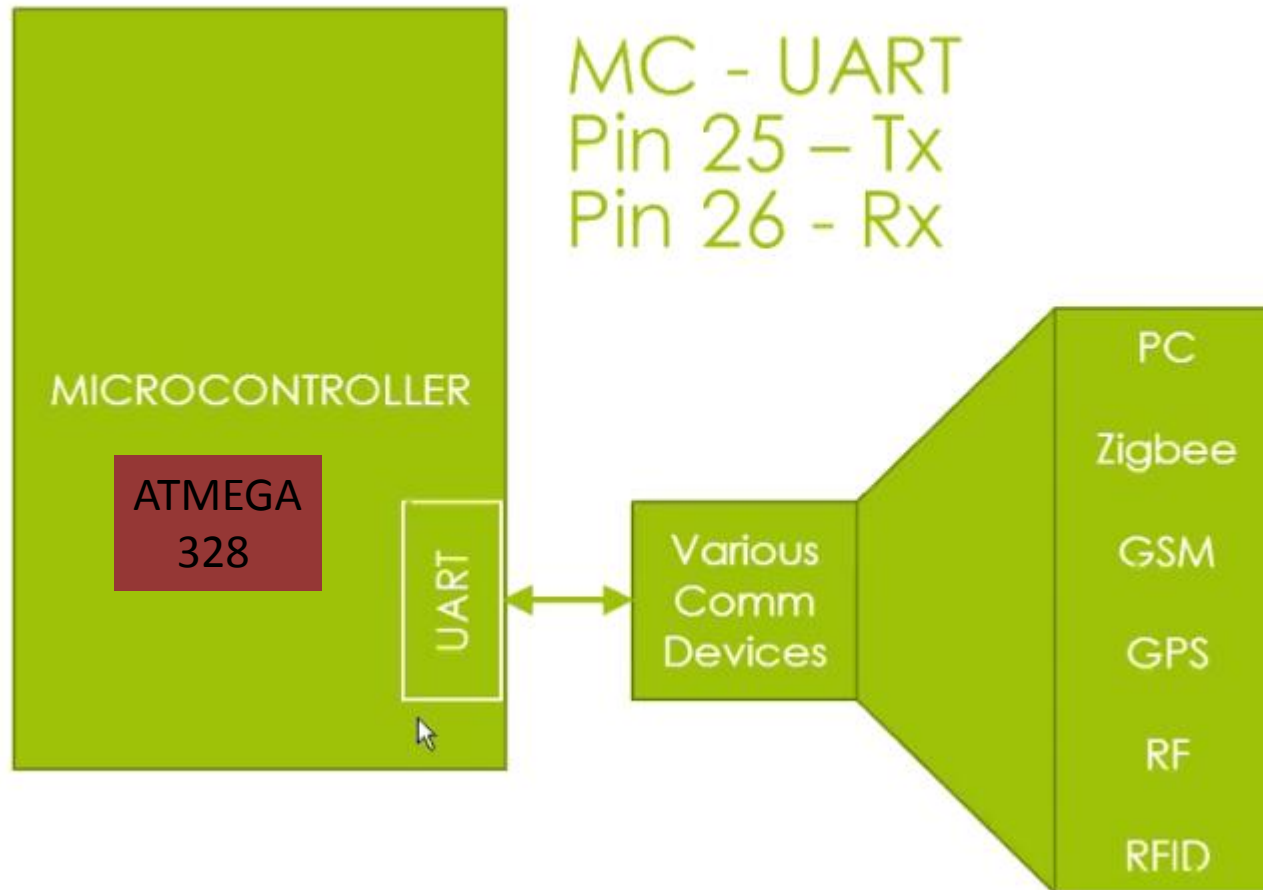

Next >> Connecting to a PC

Connecting to PC

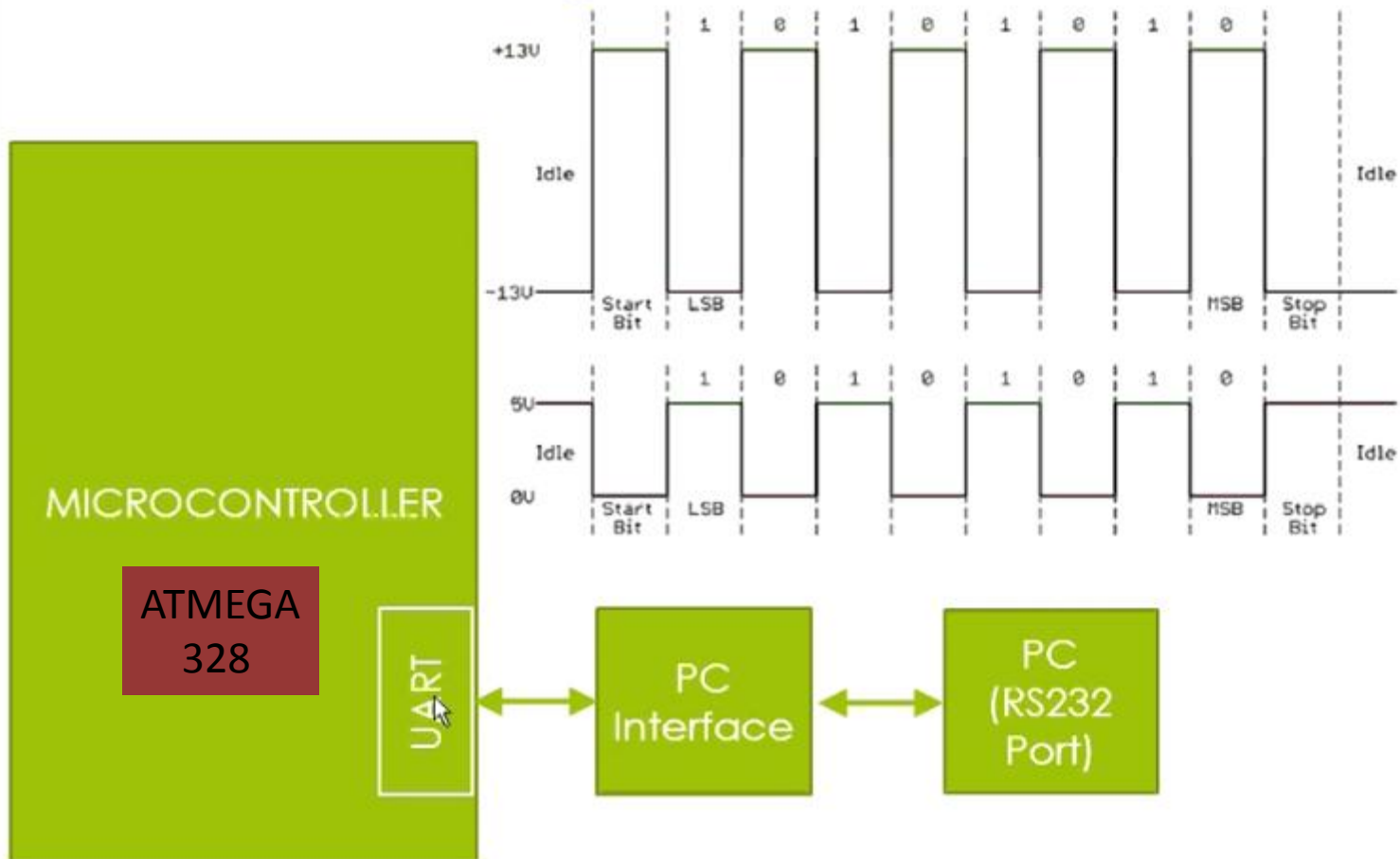


Next >> MAX232

IC MAX 232

- MAX232 is a IC that can do the function of voltage conversion.
- It is a dedicated IC meant for RS232 voltage conversions
- Manufactured by Maxim Semiconductors – hence called MAX
- Used for RS232 conversions hence MAX232
- It is a 16 Pin IC that can do voltage conversions in both direction – Tx and Rx
- Works at 5V hence very convenient to use.
- Requires some external passive components for performing the voltage conversion


Circuit Diagram

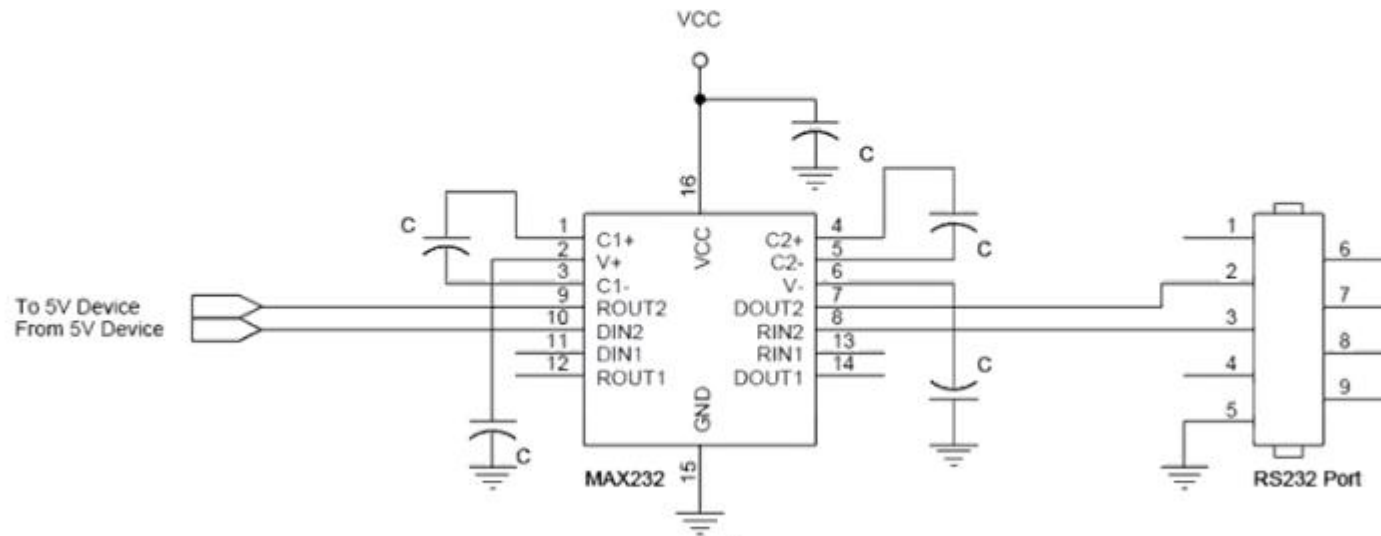

PC Interface Circuit


Xbee and Tarang F4

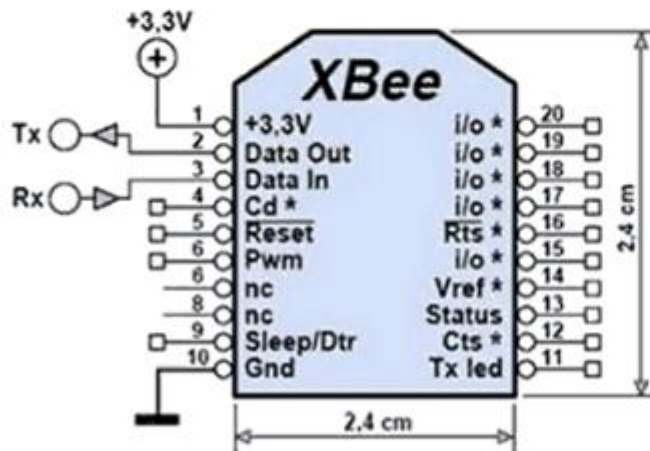- Indor Range 100 ft (30 m)
- Outdoor Range 300 ft (100 m)
- Frequency 2.4Ghz
- Supply Voltage : 3.3V DC
- 20Pin DIP Package




Next >> Connecting to MC

Connecting to Zigbee / RF Modules

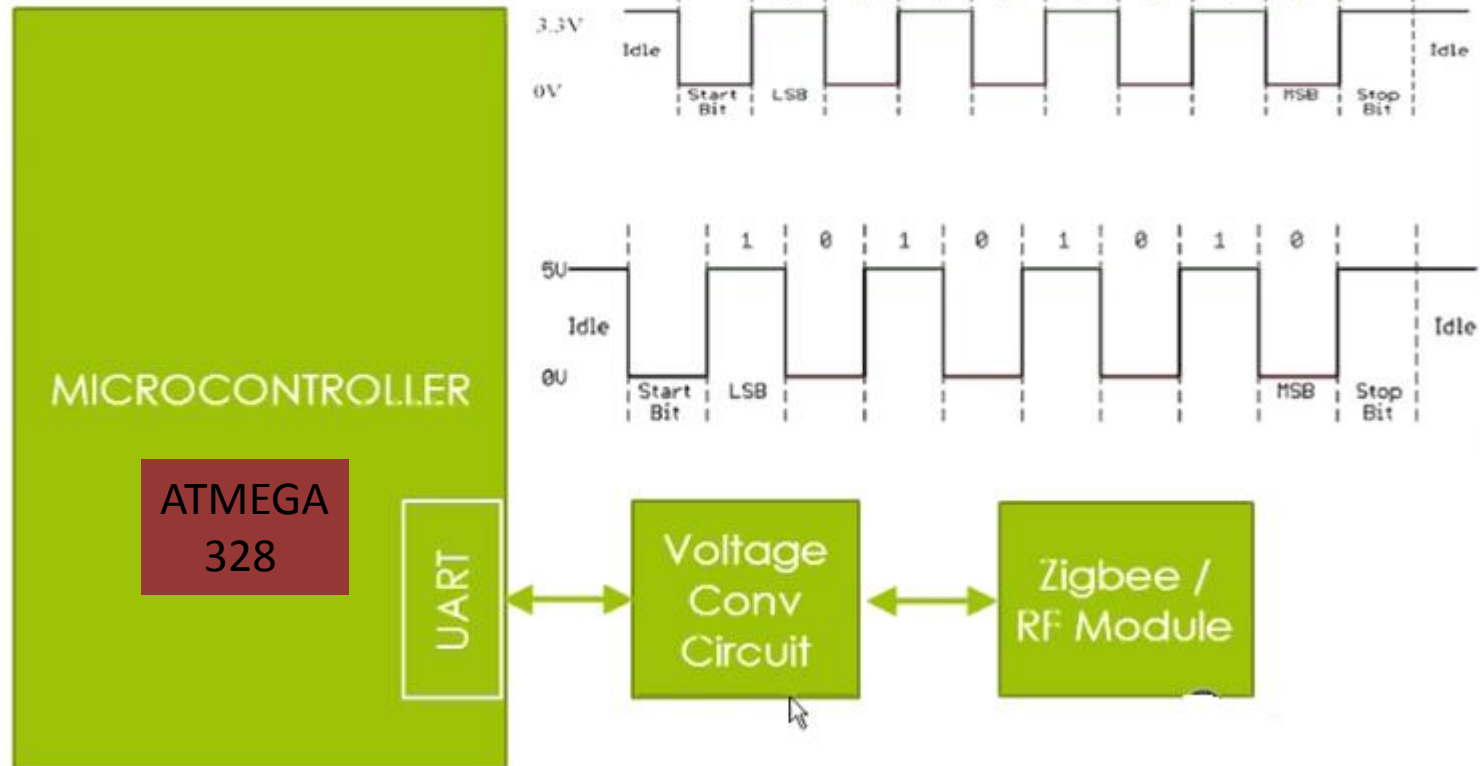


Next >> Voltage Conv Ckt

Voltage Conversion Circuit

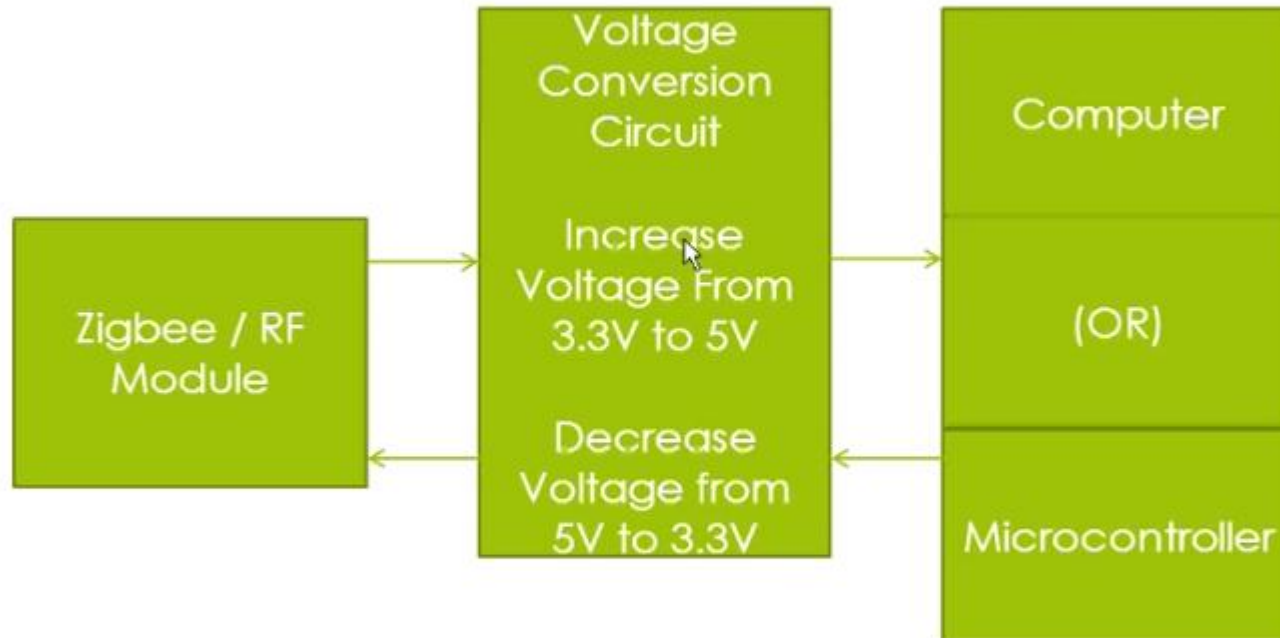

Next >> Voltage Conv Ckt


Voltage Conversion Circuit

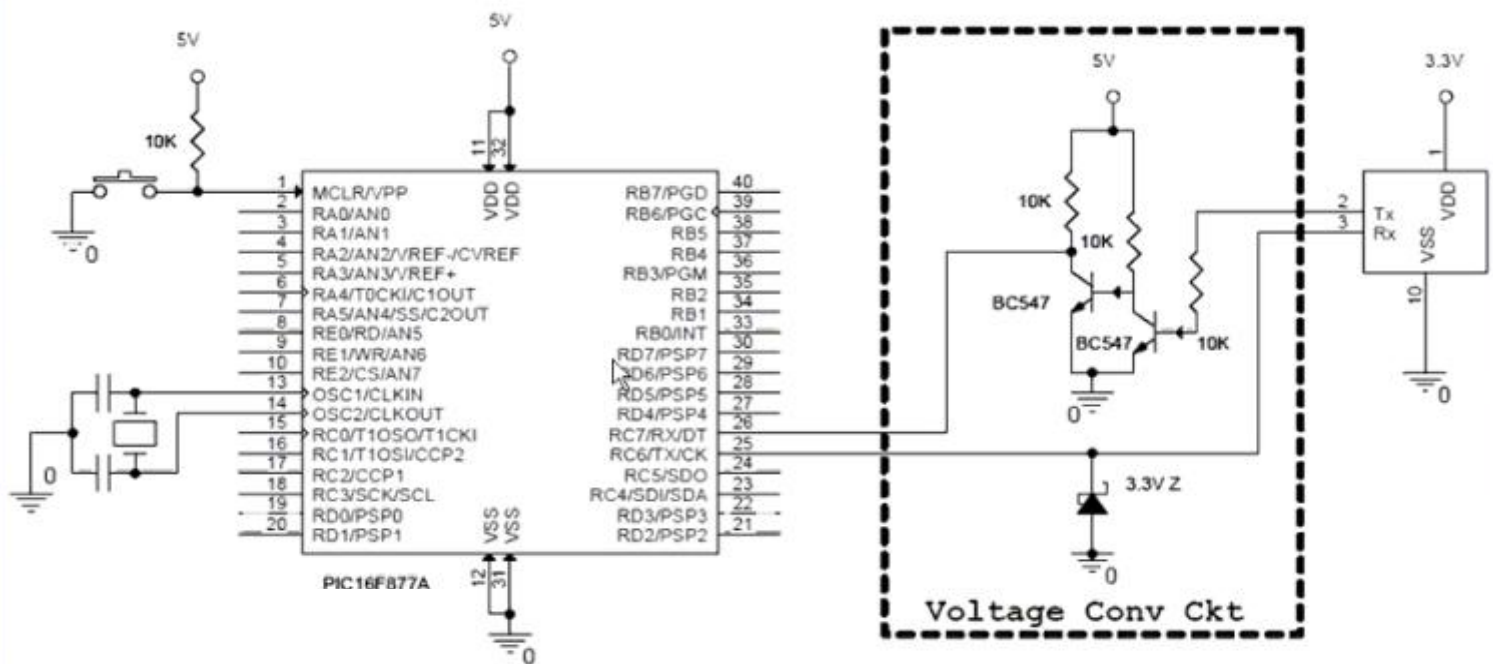

Next >> GSM / GPS / RFID


GSM / GPS / RFID

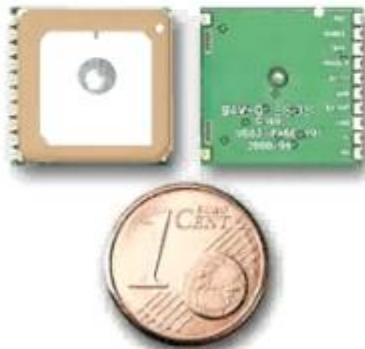- GSM : SIM900
- RFID : DT125EMUA
- GPS : RASTA-634R



Next >> Connecting to a MC


Example Circuit - GSM

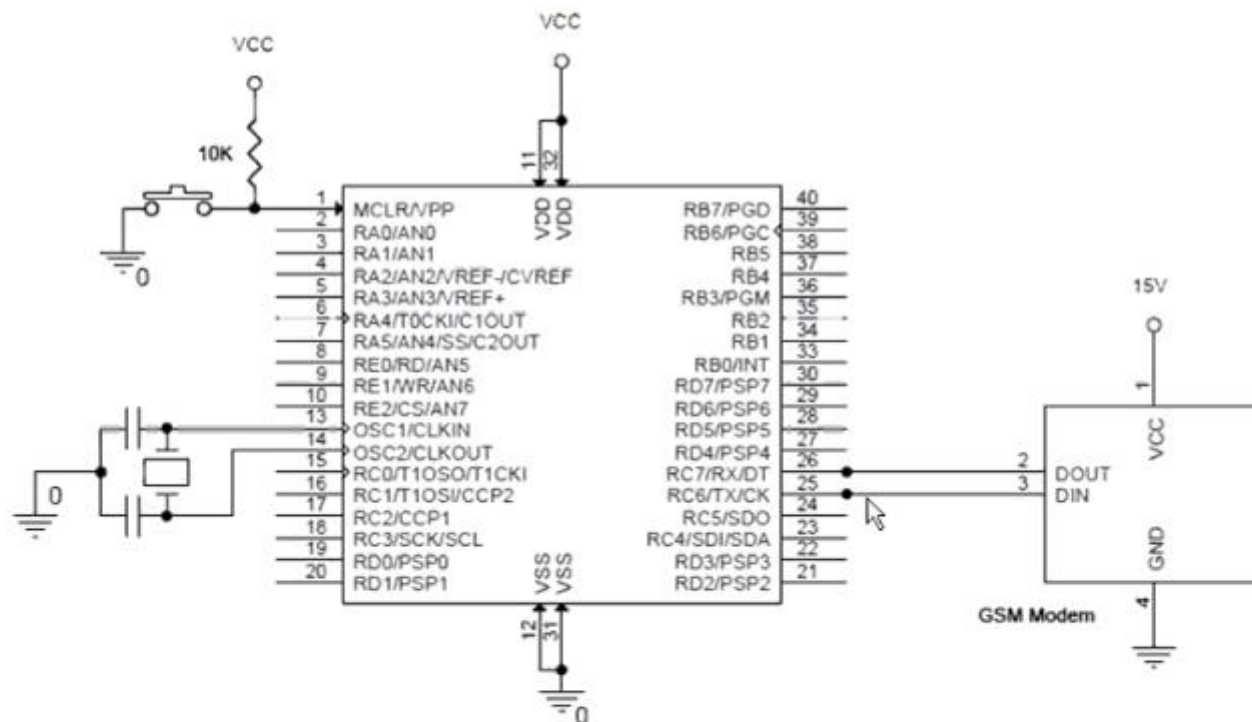

Connecting Multiple Devices

- When more than one communication device is to be connected use a multiplexer
- IC 74157 is a multiplexer used for projects.
- Using the multiplexer any combination of communication devices can be connected to the MC
- Example GSM and PC

Sensors and Analog Inputs

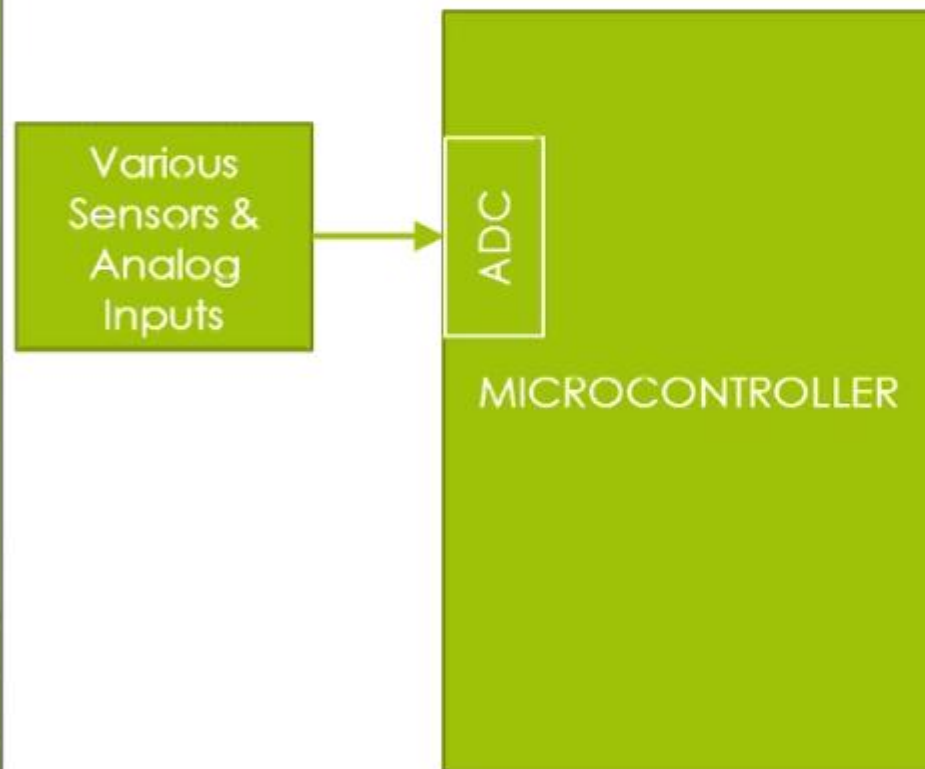


- Temperature
- Pressure
- Humidity
- Level
- IR Distance Sensors
- Gases
- LDR


Next >> Sensor Details

- Temperature – LM35
- Pressure – MPX5010
- Level – MPX5010
- Humidity – SY-HS-220
- Gases – MQ6, MQ7
- IR Distance Sensors – Sharp GP2Y0A21YK0F
- LDR

20

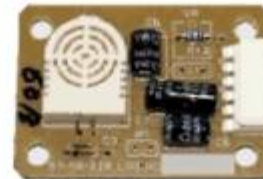

Connecting a Analog Sensor

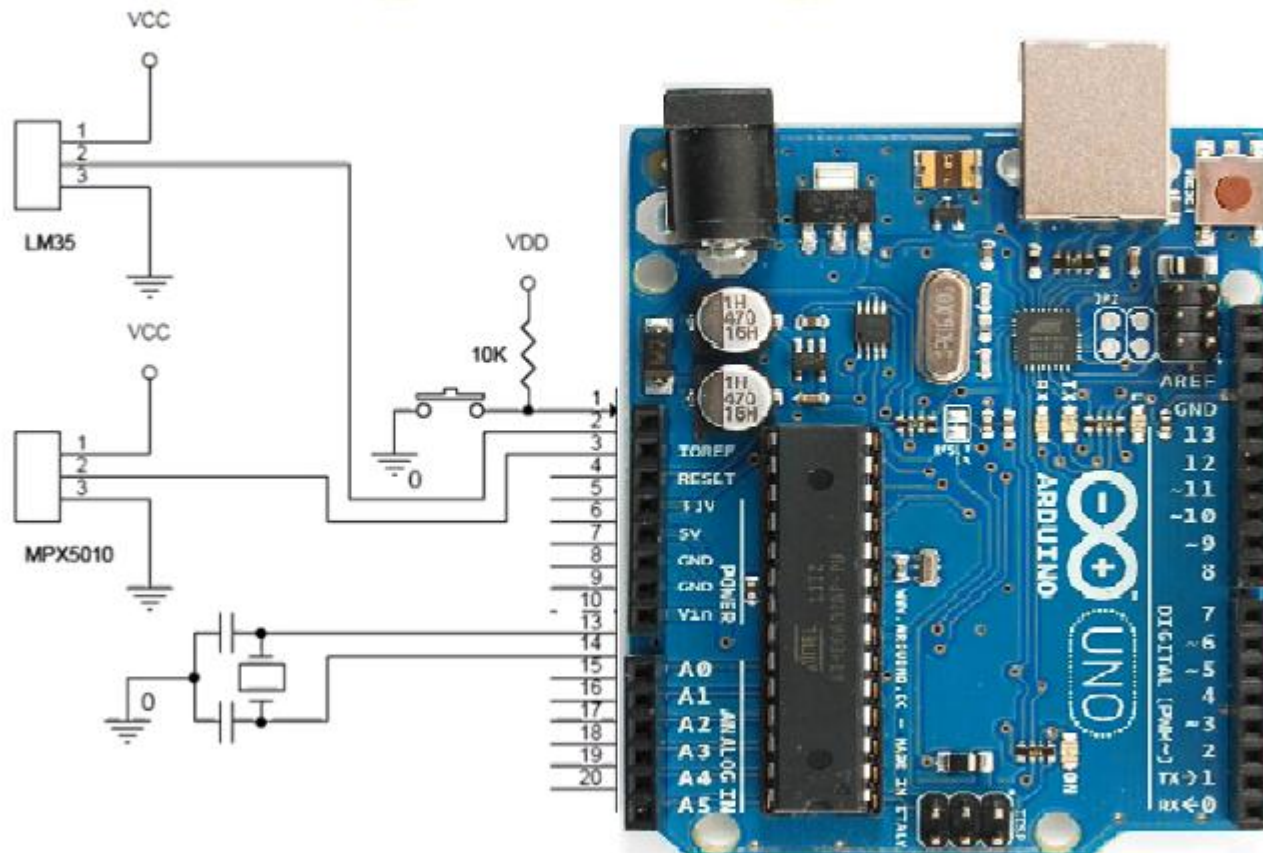

Thank You